

EEE444 Robust Feedback Theory - LabAssignment 1- Preliminary Work

Ezgi Demir, 22103304


"I completed this homework assignment independently."

Part 1 a and b)

$$V_C/C = 0.66 = v_p/c \quad C = 3.00 \times 10^8 \text{ m/s}$$

$$V_C = v_p = 0.66 \times 3 \times 10^8 \approx 1.98 \times 10^8 \text{ m/s}$$
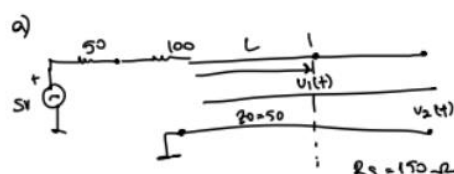
$$t_{\text{an}} = \frac{1.98 \times 10^8}{50} \approx 3.96 \times 10^6 \text{ s}$$



$$\tau = \frac{25.25 \text{ ns}}{50} \text{ (for 5m)}, \text{ for } 10\text{m} = 2L \rightarrow 50.5 \text{ ns}$$

(from now on, we call $\tau = 25.25 \text{ ns}$)

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{when } Z_L = \infty$$

$$\Gamma_L = \frac{\infty - 50}{\infty + 50} = 1 \text{ (open circuit)}$$

(load end reflection)

$$V_t = \frac{5 \cdot 50}{20 + 50} = \frac{5 \cdot 50}{70} = 1.25 \text{ V}$$

$$\Gamma_S = \frac{R_S - Z_0}{R_S + Z_0} = \frac{150 - 50}{150 + 50} = 0.5$$

(when a backward wave returns the amount of re-enters the line)

$$\text{for } V_2(t) \quad \text{when } t < 2\tau \quad V_2 = 0$$

$$\text{when } 2\tau < t < 4\tau \quad V_2 = (1.25 \text{ V})2 = 2.5 \text{ V}$$

$$\text{when } 4\tau < t < 6\tau \quad V_2 = 2(1.25 + 0.625) = 3.75 \text{ V}$$

$$0.5 \times 1.25$$

$$\text{when } 6\tau < t < 8\tau \quad V_2 = 2(1.25 + 0.625 + 0.3125) = 4.375 \text{ V}$$

$$0.5 \times 0.625$$

$$\text{when } 8\tau < t < 10\tau \quad V_2 = 2(1.25 + 0.625 + 0.3125 + 0.15625) = 4.6875 \text{ V}$$

$$3.5375 \text{ V} \quad 4.04375 \text{ V}$$

$$0.3125 \times 0.5$$

continues like that

when $t \rightarrow \infty$ approaches to 5V

when $t \rightarrow \infty$ approaches to 5V

for $V_1(t)$

first $\tau \rightarrow 2 = 5 \text{ m}$

then $3\tau \rightarrow 10 \text{ m}$, 5m returns back

$t < \tau \quad V_1 = 0$

when $0 < t < \tau \quad V_1 = 1.25 \text{ V}$

when $\tau < t < 2\tau \quad V_1 = 1.25 \text{ V} + 1.25 \text{ V} = 2.5 \text{ V}$

reflected

" $2\tau < t < 3\tau \quad V_1 = 2.5 \text{ V} + 0.625 \text{ V} = 3.125 \text{ V}$

reflected

" $3\tau < t < 4\tau \quad V_1 = 3.125 \text{ V} + 0.625 \text{ V} = 3.75 \text{ V}$


" $4\tau < t < 5\tau \quad V_1 = 3.75 \text{ V} + 0.3125 \text{ V} = 4.0625 \text{ V}$

reflected

" $5\tau < t < 6\tau \quad V_1 = 4.0625 \text{ V} + 0.15625 \text{ V} = 4.21875 \text{ V}$

refl.

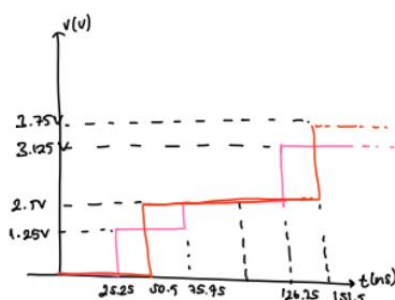continues till $t \rightarrow \infty \rightarrow$ reaches 5V



function of time (voltages of $V_1(t)$ and $V_2(t)$)

$$V_2(t) = \frac{1 - \Gamma_S (1 - \Gamma_L)^{n-1}}{1 - \Gamma_S \Gamma_L} (1.25 \text{ V}) \cdot U(t - \tau)$$

$$V_1(t) = \frac{V_2(t + T/2)}{2} + \frac{V_2(t - T/2)}{2}$$

1) b)

for $V_1(t)$:

$$\text{at } t = t_k \text{ and } t = 3t_k \rightarrow 0.5^0 \times 1.25 = 1.25V$$

$$\text{" } t = 5t_k \text{ and } t = 7t_k \rightarrow 0.5^1 \times 1.25 = 0.625V$$

$$\text{" } t = 9t_k \text{ and } t = 11t_k \rightarrow 0.5^2 \times 1.25V = 0.3125V$$

for $V_2(t)$:

$$\text{at } t = 2t_k \rightarrow 1.25V \times (1 + \Gamma_L) = 1.25 \times 2 = 2.5V$$

$$\text{at } t = 4t_k \rightarrow 1.25V \times \Gamma_S = 1.25 \times 0.5 = 0.625$$

$$\rightarrow 2\tau \rightarrow 0.625 \times (1 + \Gamma) = 0.625 \times 2 = 1.25V$$

$$\text{at } t = 6t_k \rightarrow 0.625 \times \Gamma_S \times (1 + \Gamma_L) = 0.5 \times 0.625 \times 2 = 0.625V$$

BT ... goes like that so, the corresponding plot will look like this,

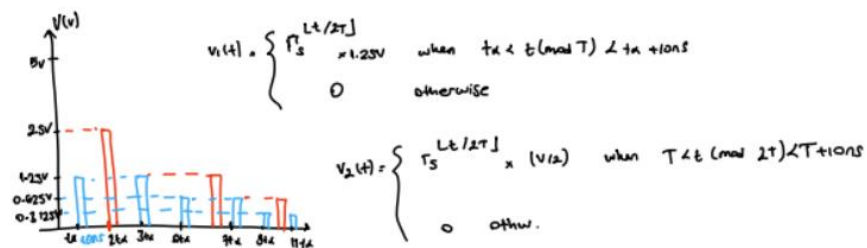


Figure 1: Part 1 Calculations and Results

Part 2

In this part I picked 280MHz, and accordingly all calculations below are made depending on this value:

2) for 21

$$\beta = \frac{\omega}{v_p} = \frac{2\pi}{\lambda} \rightarrow \beta L = \text{in radians } (\omega)$$

phase velocity

$$E = 360 \cdot \frac{l}{n_{\text{line}}} \quad n_{\text{line}} = \frac{v_f \cdot c}{f}$$

$$E = 360 \cdot \frac{8.8 \times 10^{-2}}{0.7948} \quad n_{\text{line}} \approx \frac{0.7 \times 3.00 \times 10^8}{280 \times 10^6} \approx 0.74348$$

280MHz

$$\approx 62.23^\circ$$

for 20:

$$c \approx 3.00 \times 10^8$$

$$E = 360 \cdot \frac{l}{n_{\text{line}}} \quad n_{\text{line}} = \frac{v_f \cdot c}{f}$$

$$\beta = \frac{\omega}{v_p} = \frac{2\pi}{\lambda}$$

phase velocity

$$N_{20} = 0.8 \cdot \frac{c}{f} \approx \frac{0.8 \times 3.00 \times 10^8}{280 \times 10^6} = 0.8571$$

$$E = 360 \cdot \frac{50 \times 10^{-2}}{0.8571} \approx 21.01$$

$$2\pi v_p = N \omega \rightarrow 2\pi f$$

$$v_p = N f$$

$$N = \frac{v_f}{f}$$

Figure 2: Derivations of triple stub Matching

After these values are inserted, necessary tuning operations are made according to what we are asked.

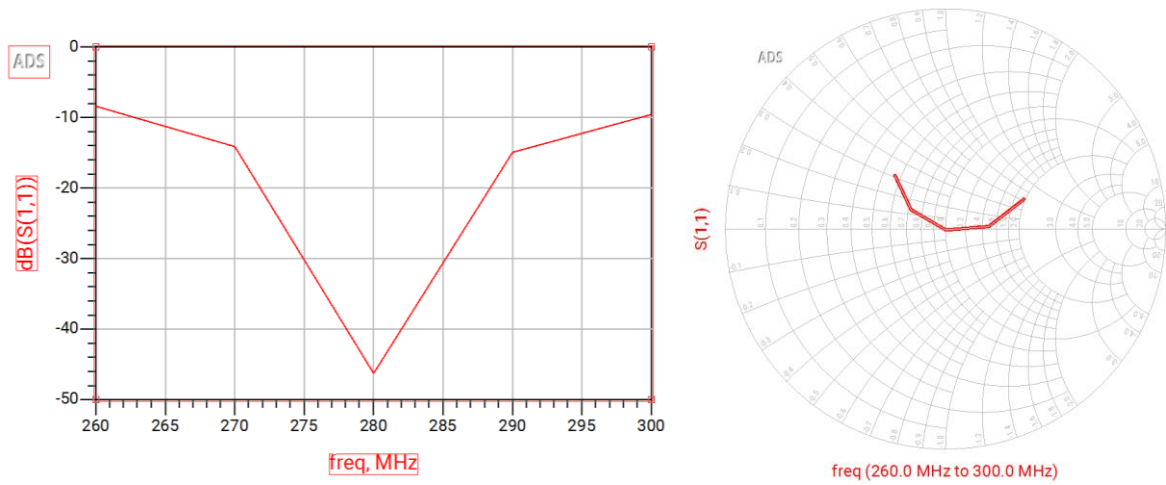


Figure 3: Tuned S11 Result at 280MHz

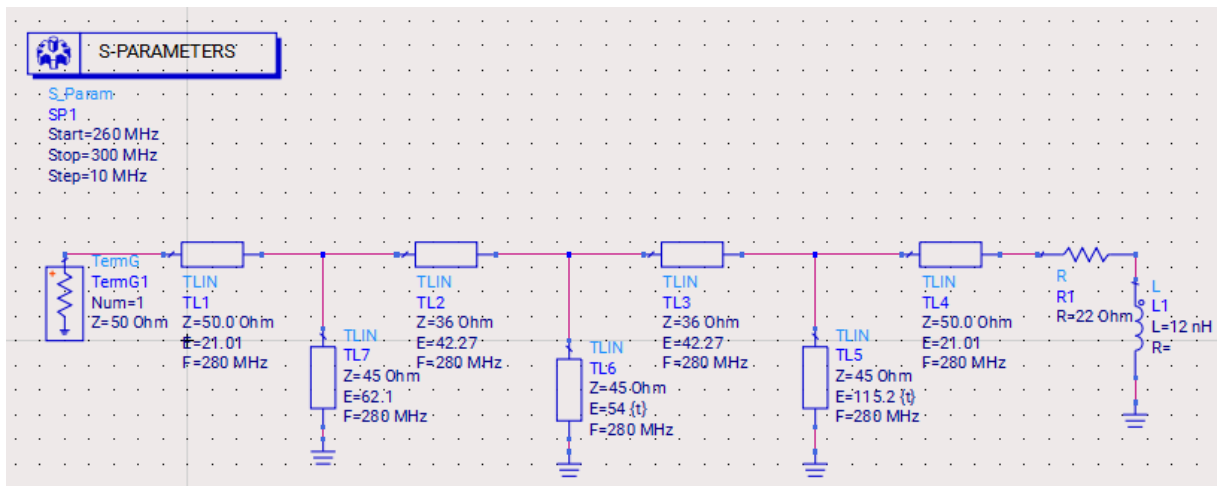


Figure 4: Tripl- strub Matching Circuit

The resulting S_{11} curve shows a deep notch at 280 MHz, which corresponds to nearly perfect matching. This confirms that the network achieves an excellent conjugate match between the $50\ \Omega$ source and the complex load. The Smith chart verifies that the impedance trajectory passes precisely through the chart center at 280 MHz, indicating zero reflection. All fixed and stub line lengths were adjusted directly in ADS to minimize S_{11} at 280 MHz, without using ideal lumped elements or theoretical simplifications.

Part 3)

- a) We are given an original microstrip LPF design. The dimensions of the microstrip lines are given in the schematic. We are asked to enter the schematic in ADS and plot the S11 and S21 of the filter.

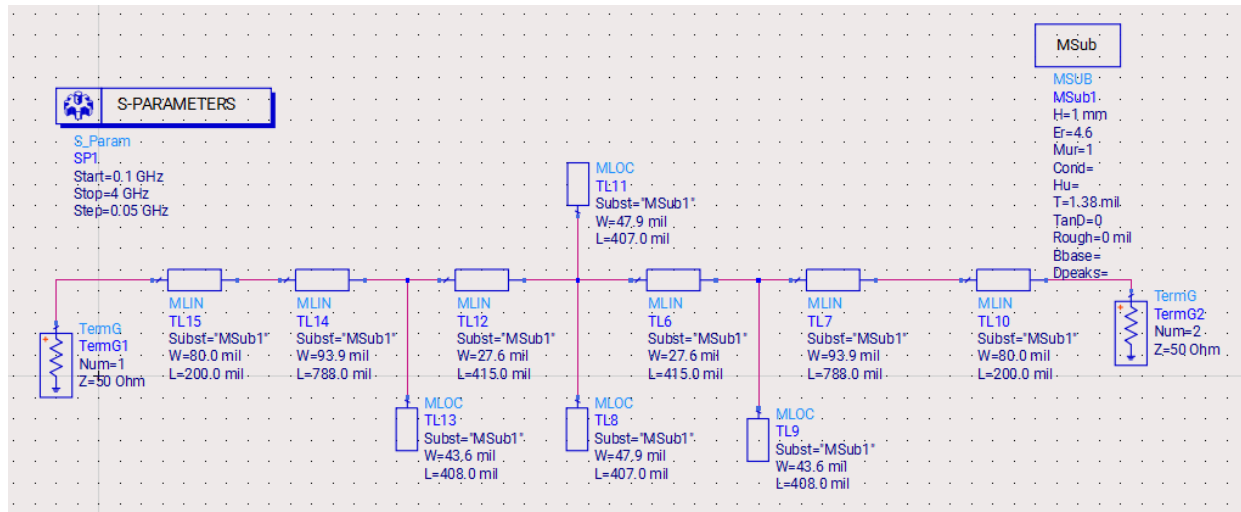


Figure 5: ADS Schematic of the Microstrip Low-pass Filter

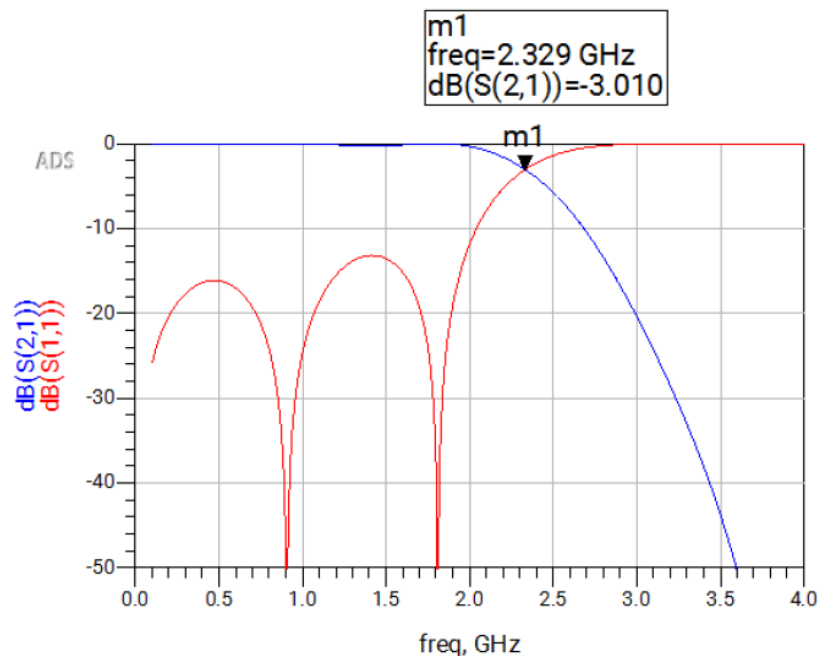


Figure 6: Microstrip Low-pass Filter Response (S11-S21)

b) In this part we modified the filter so that the corner frequency is different = 2.5GHz. Below calculations are made to find new lengths.

$$3)b) \quad 2.3 - 2.35 \text{ GHz corner freq!} \\ = f_c^{\text{fold}}$$

$$\text{I pick } f_c^{\text{new}} = 2.5 \text{ GHz}$$

$$s = \frac{2.33}{2.5} = 0.932$$

$$\text{for TL15} \rightarrow 200 \times 0.932 = 186.4 \text{ m}\lambda$$

$$\text{" TL14} \rightarrow 788 \times 0.932 = 734.416 \text{ m}\lambda$$

$$\text{" TL13} \rightarrow 408 \times 0.932 = 380.256 \text{ "}$$

$$\text{" TL12} \rightarrow 415 \times 0.932 = 386.78 \text{ "}$$

$$\text{" TL11} \rightarrow 407 \times 0.932 = 379.324 \text{ "}$$

$$\text{" TL9} \rightarrow 408 \times 0.932 = 380.256 \text{ "}$$

$$\text{" TL8} \rightarrow 407 \times 0.932 = 379.324 \text{ "}$$

$$\text{" TL7} \rightarrow 788 \times 0.932 = 734.416 \text{ "}$$

$$\text{" TL10} \rightarrow 200 \times 0.932 = 186.4 \text{ "}$$

$$\text{" TL6} \rightarrow 415 \times 0.932 = 386.78 \text{ "}$$

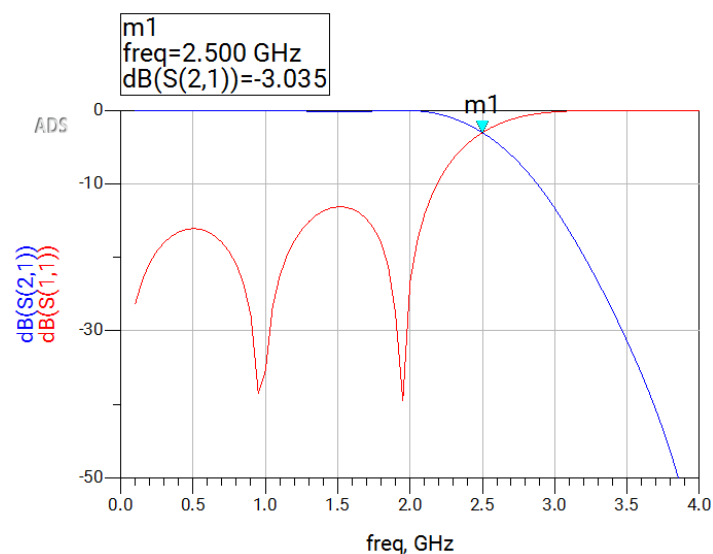


Figure 7: Microstrip Low-pass Filter Response redesigned when $f_c \approx 2.5\text{GHz}$ (S11-S21)

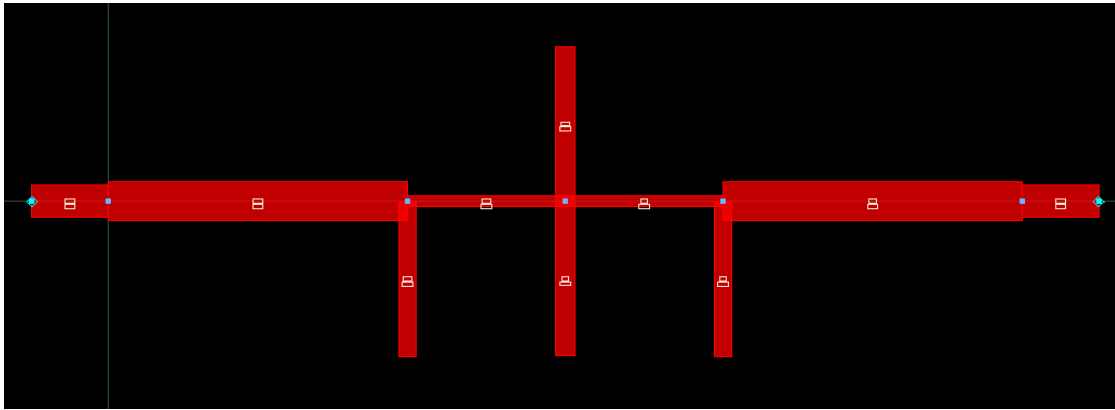


Figure 8: ADS Layout of the Low-pass Filter

Part 4)

a)

We have a microstrip band-pass filter built on the same substrate. Using the given schematic, we are asked to plot the S11 and S21 of the filter.

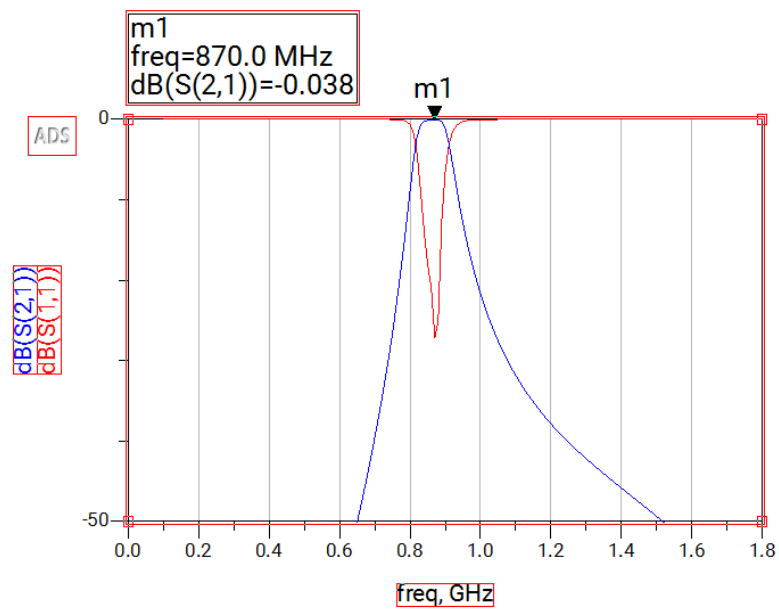


Figure 9: Microstrip BP Filter Response when $f_c \approx 870\text{MHz}$ (S11-S21)

$$|| \quad T_L 12 = 700 \times 1.16 = 812 \quad ||$$

7

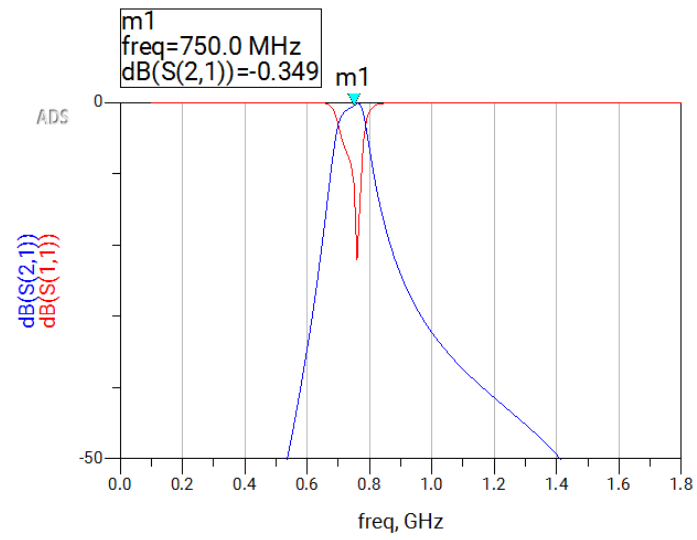


Figure 11: Scaled BPF Response When New $f_c = 750\text{MHz}$

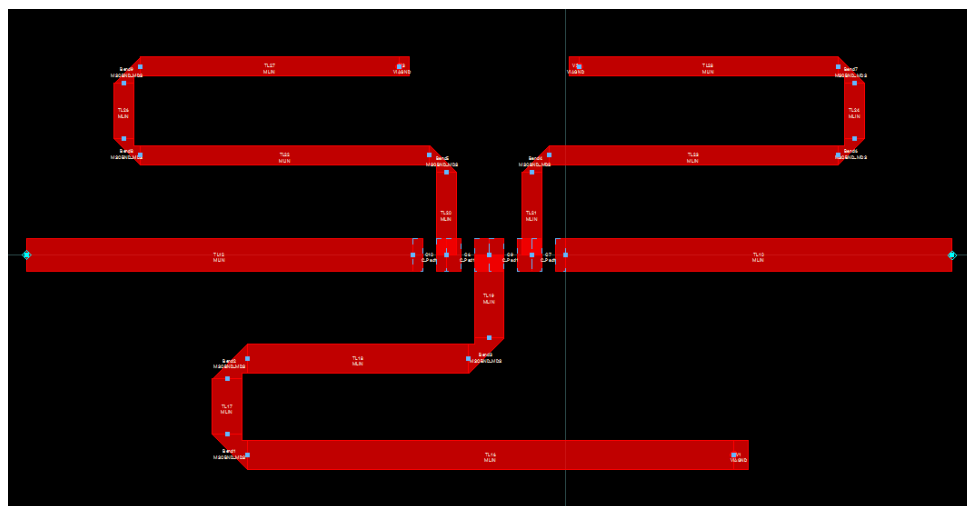


Figure 12: ADS Layout of the Band-pass Filter